

# Elektroniske enheter og kretser


## Lab 02

Sølve Kjølseth

September 18, 2025

### 0. Abstract

This lab investigated the behaviour and characteristics of a bipolar junction transistor (BJT) in Fixed-Bias and Voltage-Divider Bias configurations. Two circuits were used to determine the transistor current gain, denoted  $\beta$ , and the behaviour of the Voltage-Divider Bias configuration. Theoretical calculations were performed and compared with measured values. Using the same transistor, a Voltage-Divider Bias circuit with specific requirements was designed by calculating optimal resistor values and selecting the closest commercially available components. Measurements were then taken to evaluate the difference between the calculated circuit and actual performance. The experiment highlights the calculations, the underlying assumptions, and the agreement between theoretical predictions and experimental observations.

This report corresponds to the second lab exercise in the course. The report structure has been updated based on previous feedback, and further feedback is welcome to improve clarity and quality. All materials created for this course (L<sup>A</sup>T<sub>E</sub>X sources, images, graphs, and code) are released under the open source MIT License, and available on [GitHub](#) .

## **0.1. Table of Contents**

<b>1. Introduction</b>	<b>3</b>
<b>2. Transistor characteristics</b>	<b>4</b>
2.1. Fixed-Bias BJT Analysis . . . . .	4
2.2. Voltage and Current Verification . . . . .	5
2.3. Voltage-Divider Bias Analysis . . . . .	7
<b>3. Designing a circuit</b>	<b>11</b>
<b>4. Conclusion</b>	<b>15</b>

## **0.2. List of Figures**

2.1	Photograph of the constructed fixed-bias BJT circuit. . . . .	4
2.2	Photograph of the (incorrectly connected) Voltage-Divider Bias BJT circuit. . . . .	7
3.3	Voltage-Divider Bias BJT circuit constructed to specification. . . . .	13

## **0.3. List of Tables**

2.1	Measured values for the Fixed-Bias circuit . . . . .	4
2.2	Calculated currents and current gain . . . . .	5
2.3	Calculated voltages from the circuit analysis . . . . .	6
2.4	Measured voltages from the actual circuit . . . . .	6
2.5	Relative difference between measured and calculated voltages . . . . .	6
2.6	Measured resistance values for the Voltage-Divider Bias circuit . . . . .	8
2.7	Calculated voltages and currents for the Voltage-Divider Bias circuit . . . . .	9
2.8	Measured voltages and currents for the Voltage-Divider Bias circuit . . . . .	9
2.9	Relative difference between measured and calculated values . . . . .	10
3.10	Specifications for the circuit . . . . .	11
3.11	Calculated and chosen resistor values for the designed circuit . . . . .	12
3.12	Measurements for the designed circuit . . . . .	14
3.13	Relative difference between measured and specified values . . . . .	14

# 1. Introduction

Transistors are among the most commonly used components in electronic circuits. They serve as amplifiers, switches, and signal modulators. Even the very building blocks of modern computational electronics are transistors. One type is the bipolar junction transistor (BJT) which is explored in this experiment. A BJT has three terminals, called the collector, base, and emitter. It operates by controlling the collector current through the base current, with both currents exiting through the emitter. The most important characteristic of the BJT for this experiment is its current gain,  $\beta$ , which represents the ratio of collector current to base current. In the transistor type to be used in this experiment the gain can be several hundred, resulting in very low base currents. Understanding transistor behaviour under various resistor configurations is essential for designing circuits to specification.

The final objective of this lab is to construct a Voltage-Divider Bias BJT circuit with commercially available resistors to meet a specified design. The first objective was to determine the transistor's  $\beta$ . For determining this, a simple Fixed-Bias BJT circuit was constructed. Measurements were compared with calculations to verify the accuracy of the theoretical model. The second objective was to build a Voltage-Divider Bias BJT circuit using known resistor values, and to measure and calculate its behaviour to understand how the circuit functions. Finally, the  $\beta$  determined in the first objective and the analysis from the second objective were used to complete the final design.

This experiment demonstrates the function of a BJT and how resistor values influence circuit operation. It also highlights the practical consideration of adapting calculated ideal values to commercially available components.

## 2. Transistor characteristics

### 2.1. Fixed-Bias BJT Analysis

The first step of part 1 of the assignment is to determine the transistor's current gain  $\beta$ . The circuit shown in Figure 2.1 was constructed and the relevant measurements were recorded, summarised in Table 2.1. From these values, the base current  $I_B$  and collector current  $I_C$  are calculated using Equations 2.1 and 2.2, respectively. Finally, the transistor gain  $\beta$  is obtained using the results from the previous equations, as shown in Equation 2.3.

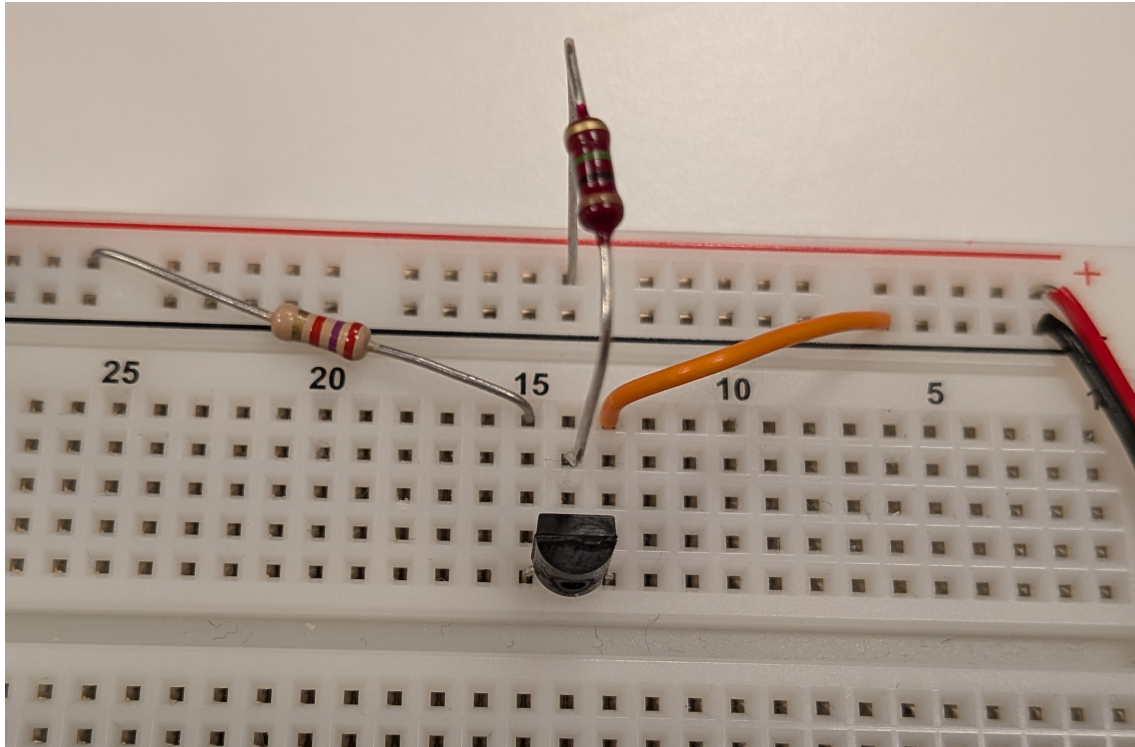


Figure 2.1: Photograph of the constructed fixed-bias BJT circuit.

Figure 2.1 shows the physical layout of the Fixed-Bias BJT circuit. The placement of the resistors and the transistor corresponds to the schematic provided in the assignment. This photograph shows the actual circuit used for measurement.

Table 2.1: Measured values for the Fixed-Bias circuit

Parameter	Value	Unit
$R_B$	997.80	$k\Omega$
$R_C$	2.76	$k\Omega$
$V_{CC}$	20.01	V
$V_{BE}$	0.68	V
$V_{RC}$	10.03	V

Table 2.1 presents the raw measurements obtained from the circuit. These values form the basis for calculating the base and collector currents.

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \quad (2.1)$$

$$I_C = \frac{V_{RC}}{R_C} \quad (2.2)$$

$$\beta = \frac{I_C}{I_B} \quad (2.3)$$

Equations 2.1–2.3 show how the base current, collector current, and transistor gain  $\beta$  are computed from the measured values.

Table 2.2: Calculated currents and current gain

Parameter	Value	Unit
$I_B$	19.37	$\mu\text{A}$
$I_C$	3.63	$\text{mA}$
$\beta$	187.45	—

Table 2.2 summarizes the calculated base and collector currents, along with the resulting transistor gain.

## 2.2. Voltage and Current Verification

Part 2 begins by calculating  $I_B$  and  $I_C$  using the measured  $\beta$  and experimental data. This step is somewhat redundant, as the currents were already determined from the measurements, so repeating the calculation yields essentially the same values with a 0 % difference.

Next, the node voltages  $V_B$ ,  $V_C$ ,  $V_E$ , and the collector-emitter voltage  $V_{CE}$  are calculated using Equations 2.4–2.6. These calculated values are summarised in Table 2.3. Note that  $V_E$  is directly connected to ground, so it is 0 V.

$$V_B = V_{CC} - (I_B \cdot R_B) \quad (2.4)$$

$$V_C = V_{CC} - (I_C \cdot R_C) \quad (2.5)$$

$$V_{CE} = V_C - V_E \quad (2.6)$$

Equations 2.4 and 2.5 give the base and collector node voltages, obtained from the voltage drops across  $R_B$  and  $R_C$  using the corresponding currents. Equation 2.6 defines the

collector-emitter voltage as the difference between  $V_C$  and  $V_E$ . The calculated values are summarised in Table 2.3.

Table 2.3: Calculated voltages from the circuit analysis

Parameter	Value	Unit
$V_B$	0.684	V
$V_C$	9.980	V
$V_E$	0.000	V
$V_{CE}$	9.980	V

These calculated voltages serve as a theoretical reference for comparison with the measurements from the physical circuit.

Table 2.4: Measured voltages from the actual circuit

Parameter	Value	Unit
$V_B$	0.683	V
$V_C$	9.970	V
$V_E$	0.000	V
$V_{CE}$	9.970	V

The measured voltages are recorded directly from the circuit. Comparing these with the calculated values allows assessment of the accuracy of the theoretical model.

$$Difference = \frac{Measured - Calculated}{Calculated} \cdot 100 \quad (2.7)$$

Equation 2.7 defines the relative percentage difference between measured and calculated voltages, providing a quantitative measure of error.

Table 2.5: Relative difference between measured and calculated voltages

Parameter	Difference %
$V_B$	-0.15
$V_C$	-0.10
$V_E$	0.00
$V_{CE}$	-0.10

The relative differences shown in Table 2.5 confirm that the measured values closely match the theoretical predictions. This comparison validates the use of the measured  $\beta$  for calculating the circuit behaviour and highlights the minimal experimental error. The

small error mainly reflects that measured rather than ideal theoretical values were used in the calculations.

### 2.3. Voltage-Divider Bias Analysis

Part 3 examines the behaviour of the transistor when configured with a Voltage-Divider Bias instead of the Fixed-Bias arrangement used previously. The constructed circuit is shown in Figure 2.2. It should be noted that the photograph was taken prior to correcting a wiring error at the base connection, which was resolved before any measurements were performed.

The resistor values were first measured, as listed in Table 2.6. Using these, approximate voltages and currents were calculated from Equations 2.8–2.14, with results shown in Table 2.7. Measurements of the actual circuit were then recorded in Table 2.8, and the calculated and measured results were compared. The outcome of this comparison is presented in Table 2.9, allowing an evaluation of how closely the theoretical model matches the real circuit.

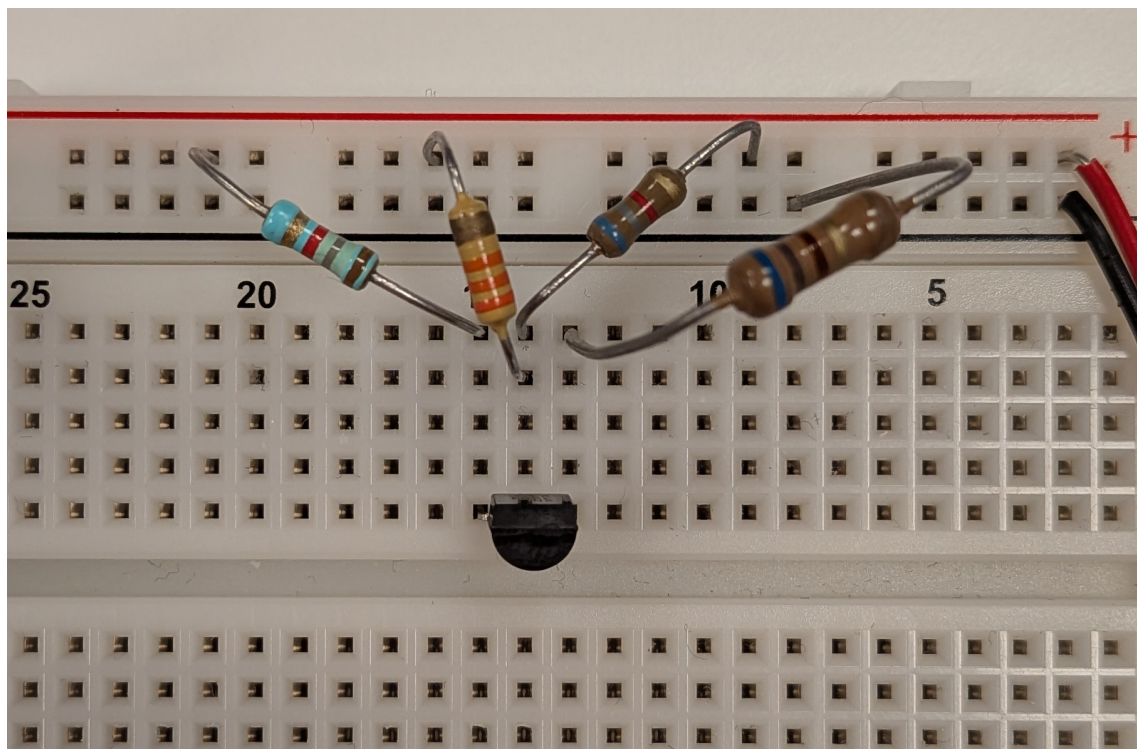


Figure 2.2: Photograph of the (incorrectly connected) Voltage-Divider Bias BJT circuit.

The resistor values of the circuit were first measured, and these results are summarised in Table 2.6. These measurements are used as the basis for the subsequent theoretical calculations.

Table 2.6: Measured resistance values for the Voltage-Divider Bias circuit

Parameter	Value	Unit
$R_1$	33.868	k $\Omega$
$R_2$	6.825	k $\Omega$
$R_C$	1.799	k $\Omega$
$R_E$	675.400	$\Omega$

From these resistance values, the node voltages and corresponding current values are estimated, along with the collector-emitter voltage drop, using Equations 2.8–2.14.

$$V_B \approx V_{CC} \cdot \frac{R_2}{R_1 + R_2} \quad (2.8)$$

Equation 2.8 provides an approximate value of the base voltage, assuming that the base current  $I_B$  is negligible compared with the current through  $R_2$ .

$$V_E = V_B - V_{BE} \quad (2.9)$$

Equation 2.9 gives the emitter voltage as the difference between the base voltage and the base-emitter drop, where  $V_{BE}$  is assumed to be 0.7 V.

$$I_E = \frac{V_E}{R_E} \quad (2.10)$$

Equation 2.10 relates the emitter current to the emitter voltage and the emitter resistance.

$$I_B = \frac{I_E}{\beta + 1} \quad (2.11)$$

$$I_C = I_B \cdot \beta \quad (2.12)$$

Equations 2.11 and 2.12 determine the base and collector currents from the emitter current and the transistor gain  $\beta$ . The value of  $\beta$  was obtained experimentally in Part 1 (Equation 2.3) and has been applied throughout these calculations.

$$V_C = V_{CC} - (I_C \cdot R_C) \quad (2.13)$$

Equation 2.13 calculates the collector node voltage from the supply voltage and the voltage drop across the collector resistor.

$$V_{CE} = V_C - V_E \quad (2.14)$$



Finally, Equation 2.14 defines the collector-emitter voltage drop as the difference between the collector and emitter node voltages.

The values obtained from these calculations are presented in Table 2.7.

Table 2.7: Calculated voltages and currents for the Voltage-Divider Bias circuit

Parameter	Value	Unit
$V_B$	3.356	V
$V_E$	2.656	V
$V_C$	12.973	V
$V_{CE}$	10.317	V
$I_E$	3.933	mA
$I_C$	3.912	mA
$I_B$	20.868	$\mu$ A

Table 2.7 summarises the theoretical values of the node voltages, collector-emitter voltage, and transistor currents derived from the Voltage-Divider Bias model.

Direct measurements of the constructed circuit were then taken, and the results are listed in Table 2.8.

Table 2.8: Measured voltages and currents for the Voltage-Divider Bias circuit

Parameter	Value	Unit
$V_B$	3.239	V
$V_E$	2.557	V
$V_C$	13.230	V
$V_{CE}$	10.670	V
$I_E$	3.790	mA
$I_C$	3.770	mA
$I_B$	20.100	$\mu$ A

Table 2.8 presents the measured values obtained directly from the circuit. Comparing these with the calculated values provides an indication of the accuracy of the theoretical model.

The relative percentage differences between measured and calculated results were determined using Equation 2.7, which was introduced in Part 2. These differences are summarised in Table 2.9.

Table 2.9: Relative difference between measured and calculated values

Parameter	Difference %
$V_B$	-3.488
$V_E$	-3.730
$V_C$	1.982
$V_{CE}$	3.424
$I_E$	-3.626
$I_C$	-3.623
$I_B$	-3.681

Table 2.9 confirms that the measured values agree closely with the theoretical predictions. All differences remain within a few percent, indicating that the simplifying assumptions used in the calculations, such as neglecting the small effect of  $I_B$  in Equation 2.8, are justified. This shows that the Voltage-Divider Bias model provides a reliable representation of the actual circuit behaviour.

The results from Parts 1 to 3 demonstrate how transistor biasing circuits can be analysed through a combination of measurement and theoretical calculation. The experiments confirmed that the approximate models, while simplified, provide results that agree closely with practical measurements, with only small deviations caused by component tolerances and non-ideal device behaviour.

These findings provide a foundation for moving beyond analysis of given circuits toward the design of new ones. By understanding how resistor networks establish bias points and how well theoretical values align with measured results, it becomes possible to select component values that achieve desired operating conditions even under real-world constraints.

### 3. Designing a circuit

Part 4 shifted from analysis of provided circuits to the design of a new Voltage-Divider Bias BJT circuit that meets specific operating conditions. The design process involves calculating theoretical resistor values, selecting the nearest commercially available components, constructing the circuit, and finally comparing the measured performance with the specified targets.

The specifications are summarised in Table 3.10, the only note is that one of the specifications is calculated in the table, where in the assignment it was specified as  $V_E = 0.1 \cdot V_{CC}$ .

Table 3.10: Specifications for the circuit

Parameter	Value	Unit
$V_{CC}$	15	V
$V_{CE}$	7.5	V
$I_C$	5	mA
$V_E$	1.5	V

The design began with calculating the collector resistor  $R_C$  using Equation 3.1.

$$R_C = \frac{V_{R_C}}{I_C} = \frac{V_{CC} - V_{CE} - V_E}{I_C} \quad (3.1)$$

The calculated value of  $R_C$  is 1.2 k $\Omega$ . The closest commercial value of 1.2 k $\Omega$  was chosen.

Next, the emitter resistor  $R_E$  is determined using Equation 3.2, where  $I_E \approx I_C$ .

$$R_E = \frac{V_E}{I_E} \approx \frac{V_E}{I_C} \quad (3.2)$$

The calculated  $R_E$  is 300  $\Omega$ . A commercial resistor of 270  $\Omega$  was selected. This value is preferred over 330  $\Omega$  because the real emitter current  $I_E$  will be slightly larger than  $I_C$  due to the base current  $I_B$ , meaning the calculated value of 300  $\Omega$  slightly overestimates the ideal resistor. Choosing 270  $\Omega$  ensures that the actual  $R_E$  is closer to the design specification.

The base voltage approximation is set using the voltage-divider formed by  $R_1$  and  $R_2$  as done in Equation 2.8. For the voltage-divider approximation to be valid, the inequality  $\beta \cdot R_E > 10 \cdot R_2$  must be satisfied, ensuring that the base current drawn by the transistor has minimal effect on the voltage at the base.  $V_B$  can be expressed as the sum of emitter voltage and the base-emitter voltage drop as seen in Equation 3.3.

$$V_B = V_E + V_{BE} \approx V_E + 0.7 \text{ V} \quad (3.3)$$

Assuming the value of 0.7 V for the base-emitter voltage drop and combining with Equation 2.8, an expression with only  $R_1$  and  $R_2$  as not known quantities can be made, as shown in Equation 3.4. This can then be rewritten to find the ratio between  $R_1$  and  $R_2$  in Equation 3.5.

$$V_E - 0.7 \text{ V} \approx V_{CC} \cdot \frac{R_2}{R_1 + R_2} \quad (3.4)$$

$$\frac{R_1}{R_2} = \frac{V_{CC}}{V_E + V_{BE}} - 1 = \frac{12.8}{2.2} \approx 5.81 \quad (3.5)$$

The maximum value of  $R_2$  is found by solving the inequality that validates the voltage-divider model as shown in Equation 3.6.

$$R_2 \leq \frac{\beta \cdot R_E}{10} \quad (3.6)$$

The resulting maximum value of  $R_2$  is 5.061 k $\Omega$ . The closest commercial value, less than this is 4.7 k $\Omega$  and is the one selected for  $R_2$ . Using the ratio from Equation 3.5 and the chosen value for  $R_2$ ,  $R_1$  is calculated as seen in Equation 3.7.

$$R_1 = R_2 \cdot \frac{12.8}{2.2} \quad (3.7)$$

The calculated value for  $R_1$  is 27.345 k $\Omega$  and the nearest commercial value of 27 k $\Omega$  was selected to be used for  $R_1$ . A summary of all calculated and chosen values is found in Table 3.11

Table 3.11: Calculated and chosen resistor values for the designed circuit

Parameter	Calculated	Chosen	Unit
$R_C$	1.200	1.200	k $\Omega$
$R_E$	0.300	0.270	k $\Omega$
$R_2$	5.061	4.700	k $\Omega$
$R_1$	27.345	27.000	k $\Omega$

The circuit was then constructed using the chosen resistor values as shown in Figure 3.3.

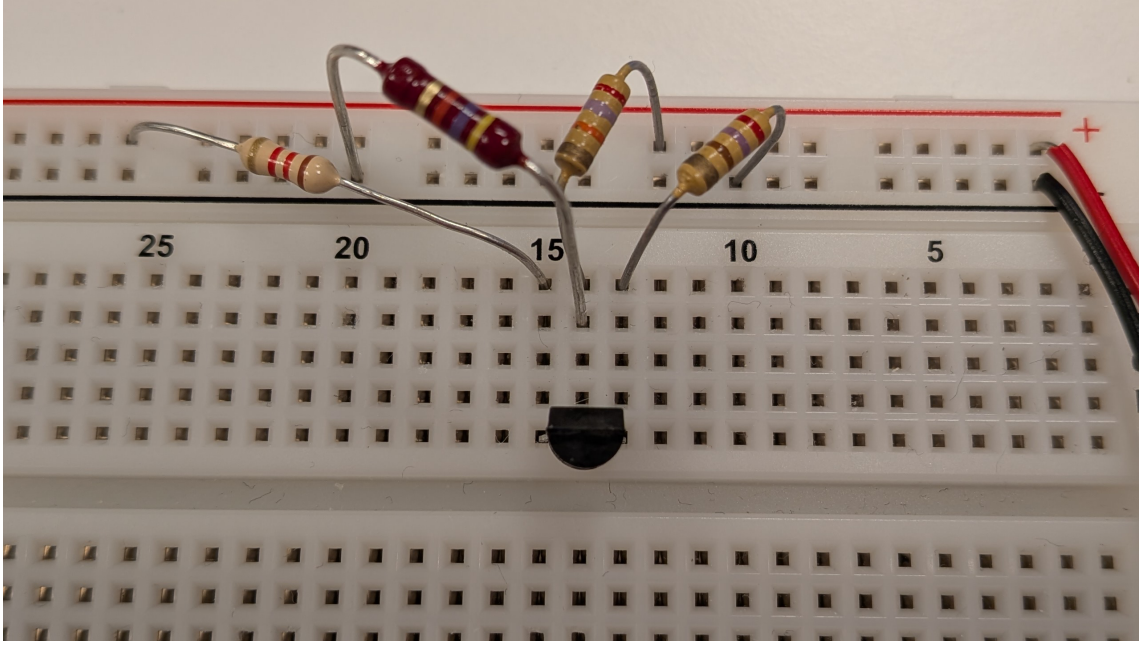


Figure 3.3: Voltage-Divider Bias BJT circuit constructed to specification.

The voltage over  $R_C$  and its resistance is measured. Then using these values the current  $I_C$  is calculated as shown in Equation 3.8

$$I_C = \frac{V_{R_C}}{R_C} \quad (3.8)$$

Voltages across  $R_1$  and  $R_2$  and the resistor values were measured accurately. Using the measured values, the divider currents are calculated in Equation 3.9.

$$I_1 = \frac{V_{R_1}}{R_1}, \quad I_2 = \frac{V_{R_2}}{R_2} \quad (3.9)$$

Using the values for the divider currents from Equation 3.9, the base current can be calculated as shown in Equation 3.10.

$$I_B = I_2 - I_C \quad (3.10)$$

When both the base and collector currents are known, the  $\beta$  can be calculated the same way as in part 1, using Equation 2.3. The emitter voltage  $V_E$  is also calculated from taking the measured supply voltage subtracting the voltage drops  $V_{R_C}$  and  $V_{CE}$  as shown in Equation 3.11.

$$V_E = V_{CC} - V_{R_C} - V_{CE} \quad (3.11)$$

All the measured values, and the calculated values that are based on measurements can be found summarised in Table 3.12

Table 3.12: Measurements for the designed circuit

Parameter	Value	Unit
$R_C$	1.186	$k\Omega$
$R_E$	0.273	$k\Omega$
$R_1$	27.306	$k\Omega$
$R_2$	4.679	$k\Omega$
$V_{CC}$	15.06	V
$V_{R_C}$	6.00	V
$V_{CE}$	7.64	V
$V_E$	1.42	V
$V_{R_1}$	12.96	V
$V_{R_2}$	2.093	V
$I_C$	5.078	mA
$I_B$	27.34	$\mu A$
$I_1$	474.6	$\mu A$
$I_2$	447.3	$\mu A$
$\beta$	131	—

The four values in the specification are compared with the actual circuit, and in addition the  $\beta$  calculated here is compared to the  $\beta$  found in part 1. The differences were calculated with Equation 2.7, where "measured" is the values found here, and "calculated" is the specification and the earlier found  $\beta$ . The results are placed in Table 3.13

Table 3.13: Relative difference between measured and specified values

Parameter	Difference %
$V_{CC}$	0.40
$V_{CE}$	1.87
$I_C$	1.56
$V_E$	-5.33
$\beta$	-0.92

The measured currents and voltages confirm that the designed circuit closely meets the specified operating conditions. Minor differences are attributed to standard component tolerances and the non-ideal characteristics of the transistor. The largest variation is in  $V_E$ , which is probably because the chosen resistor was the furthest from any calculation, laying in the middle of two commercially available values.

## 4. Conclusion

This experiment examined BJT operation in Fixed-Bias and Voltage-Divider Bias configurations, progressing from measurement and analysis to circuit design.

In the Fixed-Bias circuit, the transistor gain  $\beta$  was determined and used to validate the theoretical model. Calculated and measured values showed excellent agreement, confirming the reliability of the approach.

The Voltage-Divider Bias circuit illustrated how approximate methods can accurately predict circuit behaviour. Small deviations between theory and practice were within expected tolerances and mainly due to component variations and calculation approximations.

Finally, the experimentally determined  $\beta$  and the insights from the Voltage-Divider analysis were applied to design a circuit meeting specified conditions using commercially available resistors. The built circuit performed close to the target values, with only minor differences that reflected practical design choices.

Overall, the results show that simplified transistor models provide accurate guidance for both analysis and design, while also highlighting the need to account for tolerances when moving from theory to implementation.