

Elektroniske enheter og kretser


Lab 01

Sølve Kjølseth

September 8, 2025

0. Introduction

This is the first report in this course, detailing the completion of the first lab exercise.

Note: As always, the \LaTeX file and all other assets, such as text, images, graphs and code made by me for this project is open source with the MIT licence, see [my GitHub](#) 

0.0. Table of Contents

1. Part 1 - Diode test	3
2. Part 2 - Forward-bias characteristics	4

0.1. List of Figures

1.0 Diode being measured	3
2.0 Part 2 circuit	4
2.1 Plot of forward-bias characteristics	5

0.2. List of Tables

1.0 Diode measurments	3
---------------------------------	---

1. Part 1 - Diode test

This Part is about testing a diode characteristics with a multimeter. This means it is inherently not perfect, but it will function as a reference measurement.

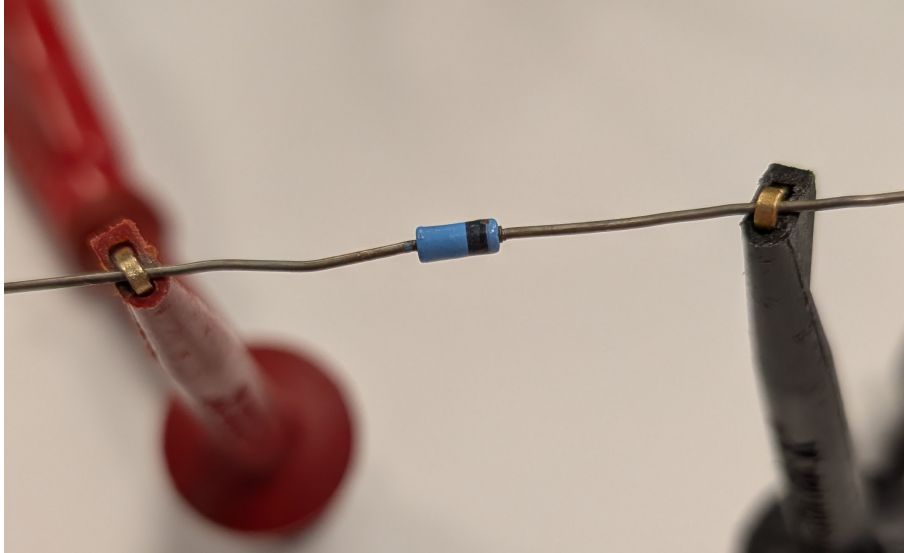


Figure 1.0: Diode being measured

Table 1.0: Diode measurements

Voltage forward	0.593 V	Resistance forward	225400 Ω
Voltage reverse	OL	Resistance reverse	OL

2. Part 2 - Forward-bias characteristics

This Part is about testing the diode characteristics for forward-bias. The values were stored in a table (RAW data like this is found on the [GitHub](#)) and then a plot was made to compare the current through the diode I_D with the voltage drop over the diode V_D .

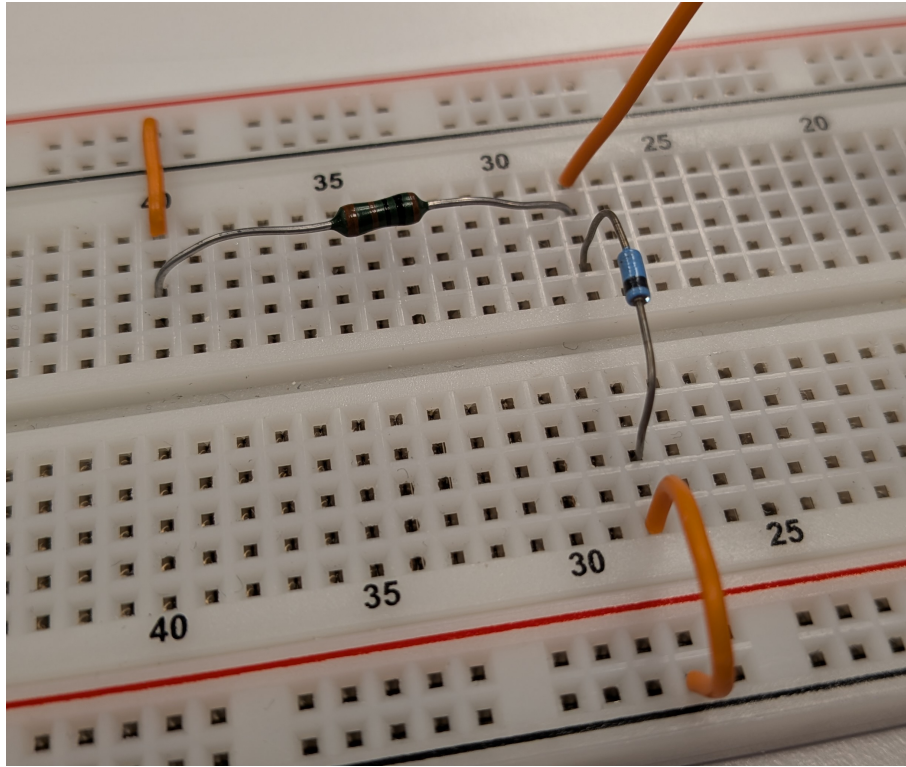


Figure 2.0: Part 2 circuit

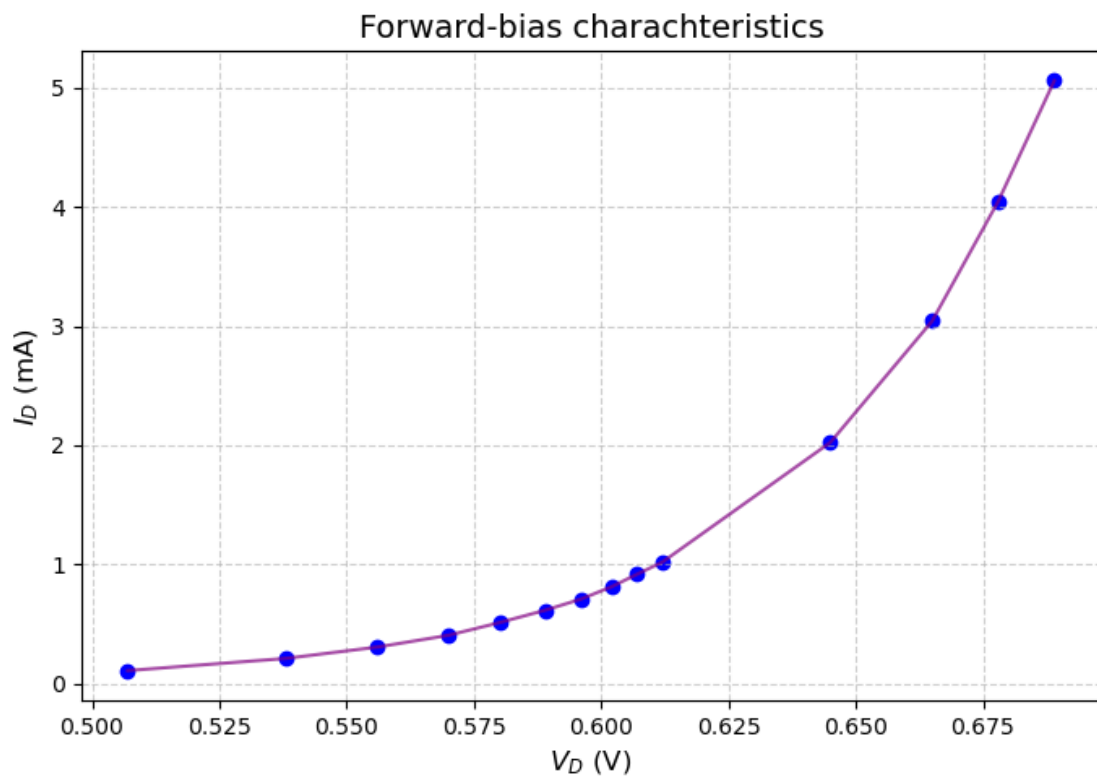


Figure 2.1: Plot of forward-bias characteristics