

# Elektroniske enheter og kretser

## Lab 01

Sølve Kjelseth

September 9, 2025

### 0. Introduction

This is the first report in this course, detailing the completion of the first lab exercise.

Note: As always, the L<sup>A</sup>T<sub>E</sub>X file and all other assets, such as text, images, graphs and code made by me for this project is open source with the MIT licence, see [my GitHub](#) 

## **0.0. Table of Contents**

<b>1. Part 1 - Diode test</b>	<b>3</b>
<b>2. Part 2 - Forward-bias characteristics</b>	<b>4</b>
<b>3. Part 3 - Reverse-bias</b>	<b>7</b>
<b>4. Part 4 - LED characteristics</b>	<b>9</b>
<b>5. Part 5 - Zener characteristics</b>	<b>11</b>

## **0.1. List of Figures**

1.0 Diode being measured . . . . .	3
2.0 Part 2 circuit . . . . .	4
2.1 Plot of forward-bias characteristics . . . . .	5
2.2 Extended plot of forward-bias characteristics . . . . .	6
3.0 Part 3 circuit . . . . .	7
4.0 Part 4 circuit . . . . .	9
4.1 Part 4 circuit . . . . .	10

## **0.2. List of Tables**

1.0 Diode measurements . . . . .	3
3.0 Reverse-bias measurements . . . . .	8
4.0 LED measurements . . . . .	10
4.1 LED values . . . . .	10

## 1. Part 1 - Diode test

This Part is about testing a diode characteristics with a multimeter. This means it is inherently not perfect, but it will function as a reference measurement.

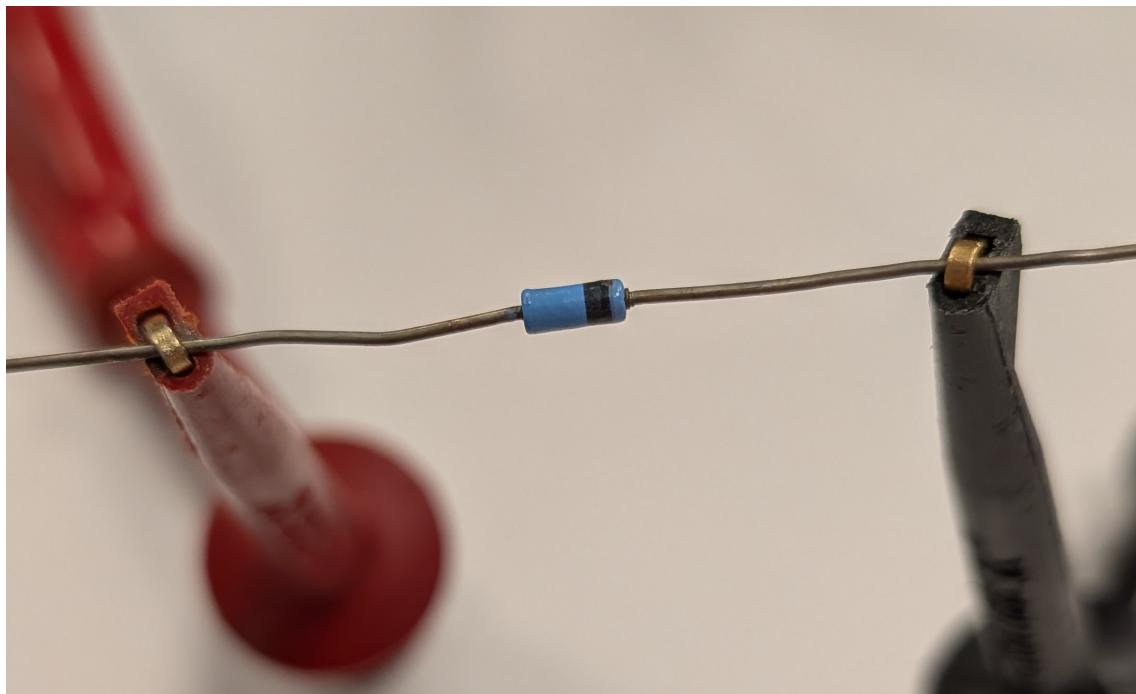


Figure 1.0: Diode being measured

Table 1.0: Diode measurements

Voltage forward	0.593 V	Resistance forward	225400 Ω
Voltage reverse	0L	Resistance reverse	0L

Interesting to note that the measured resistance in forward-bias of the diode fluctuated a lot. It went into high  $M\Omega$  to low tens of  $k\Omega$ . It was most stable around  $200\text{ k}\Omega$  and one of these measurements was therefore noted down. This could be because the multimeter is acting as a powersupply in resistance measuring mode and depending on the voltage chosen by the autoranging multimeter the diode behaviour differs.

## 2. Part 2 - Forward-bias characteristics

This Part is about testing the diode characteristics for forward-bias. The values was stored in a table (RAW data like this is found on the [GitHub](#)) and then a plot was made to compare the current through the diode  $I_D$  with the voltage drop over the diode  $V_D$ .

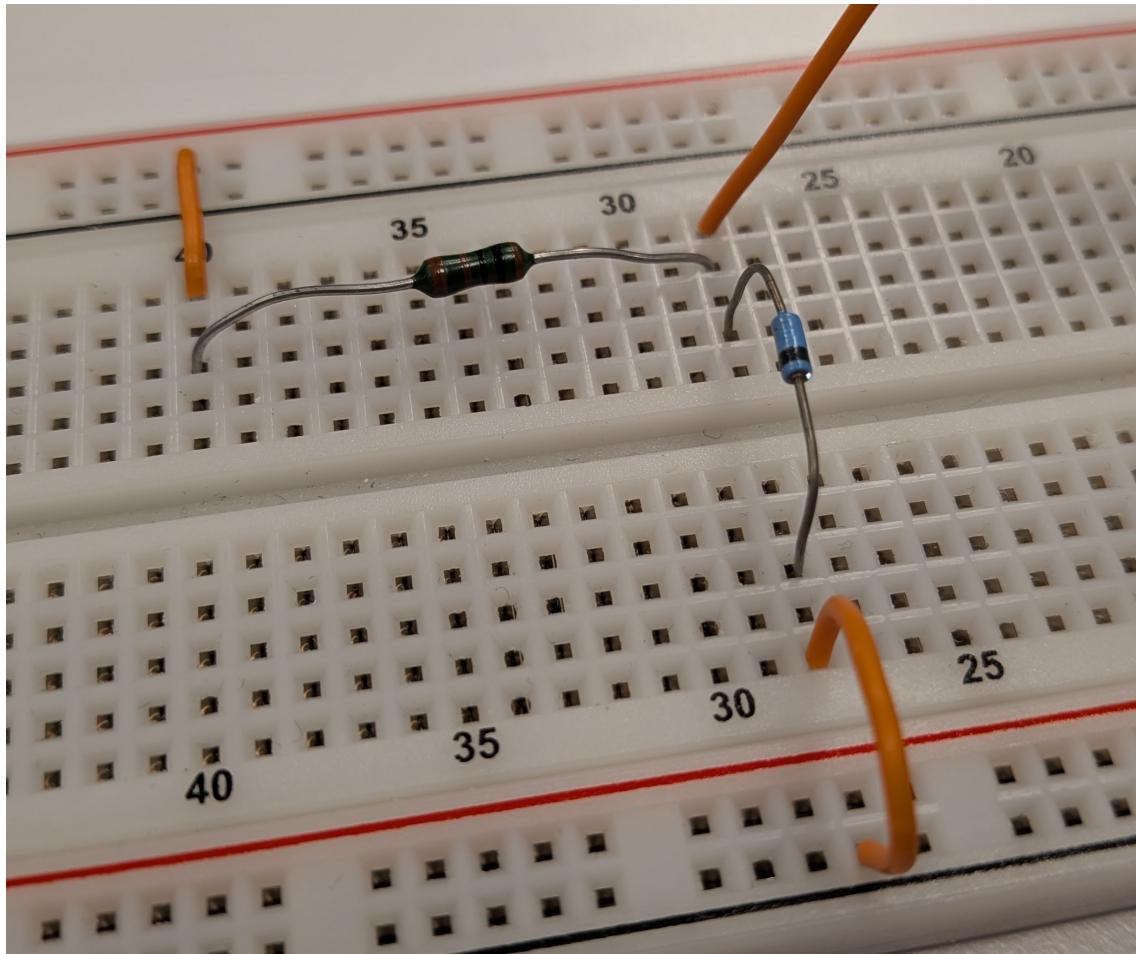


Figure 2.0: Part 2 circuit

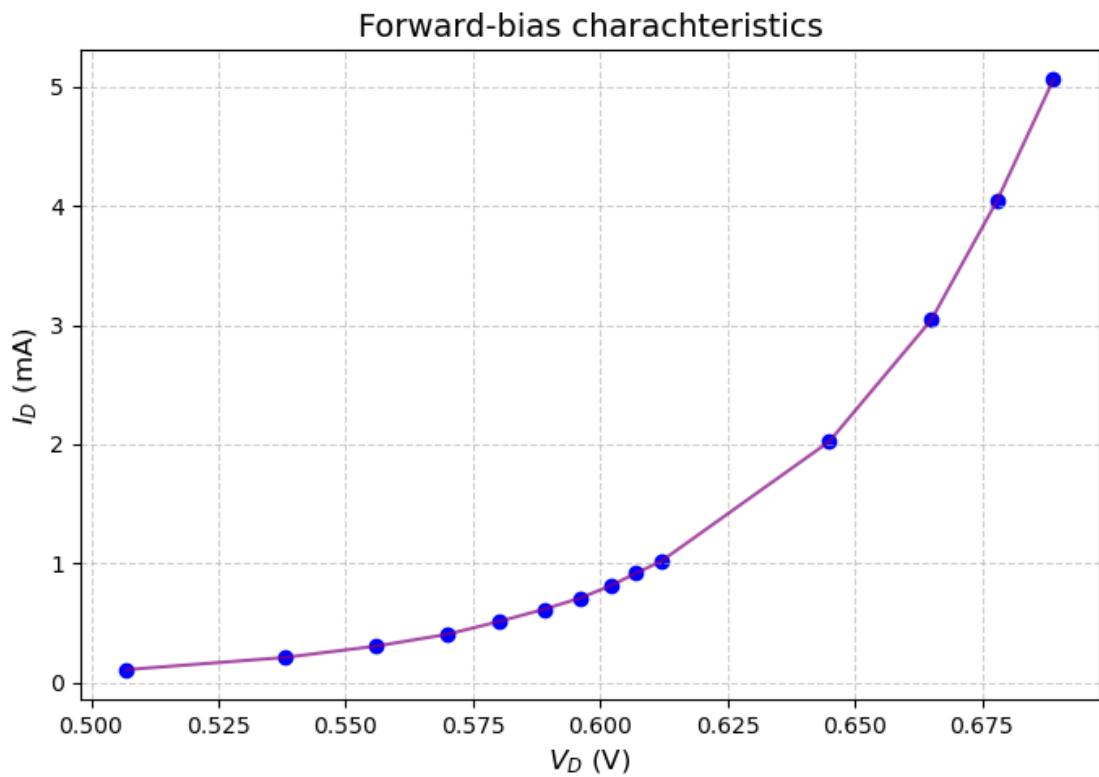


Figure 2.1: Plot of forward-bias characteristics

Now when extending the plot all the way to the origin it gets a characteristic that looks a lot different. As seen in Figure 2.2 it looks like after the initial curve the value gets linear.

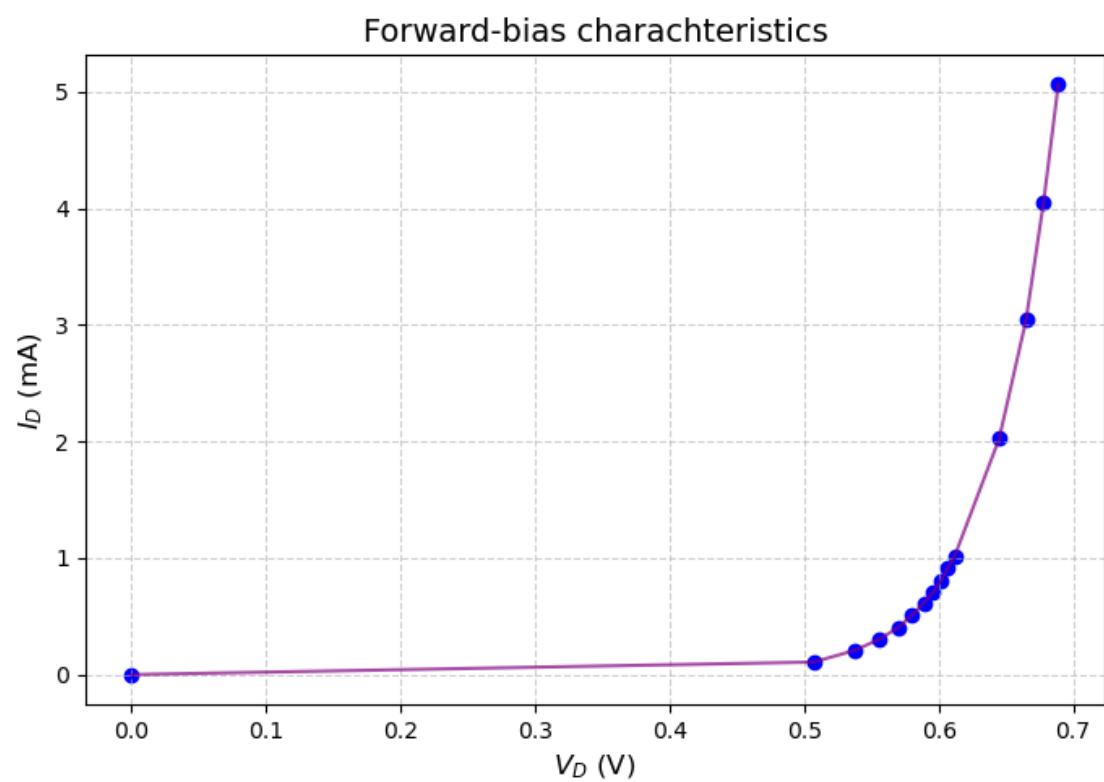


Figure 2.2: Extended plot of forward-bias charachteristics

### 3. Part 3 - Reverse-bias

This Part is about testing the reverse-bias current. Measurements were made and noted in the table, note that the assumed resistive value of the voltmeter is specified by the assignment.

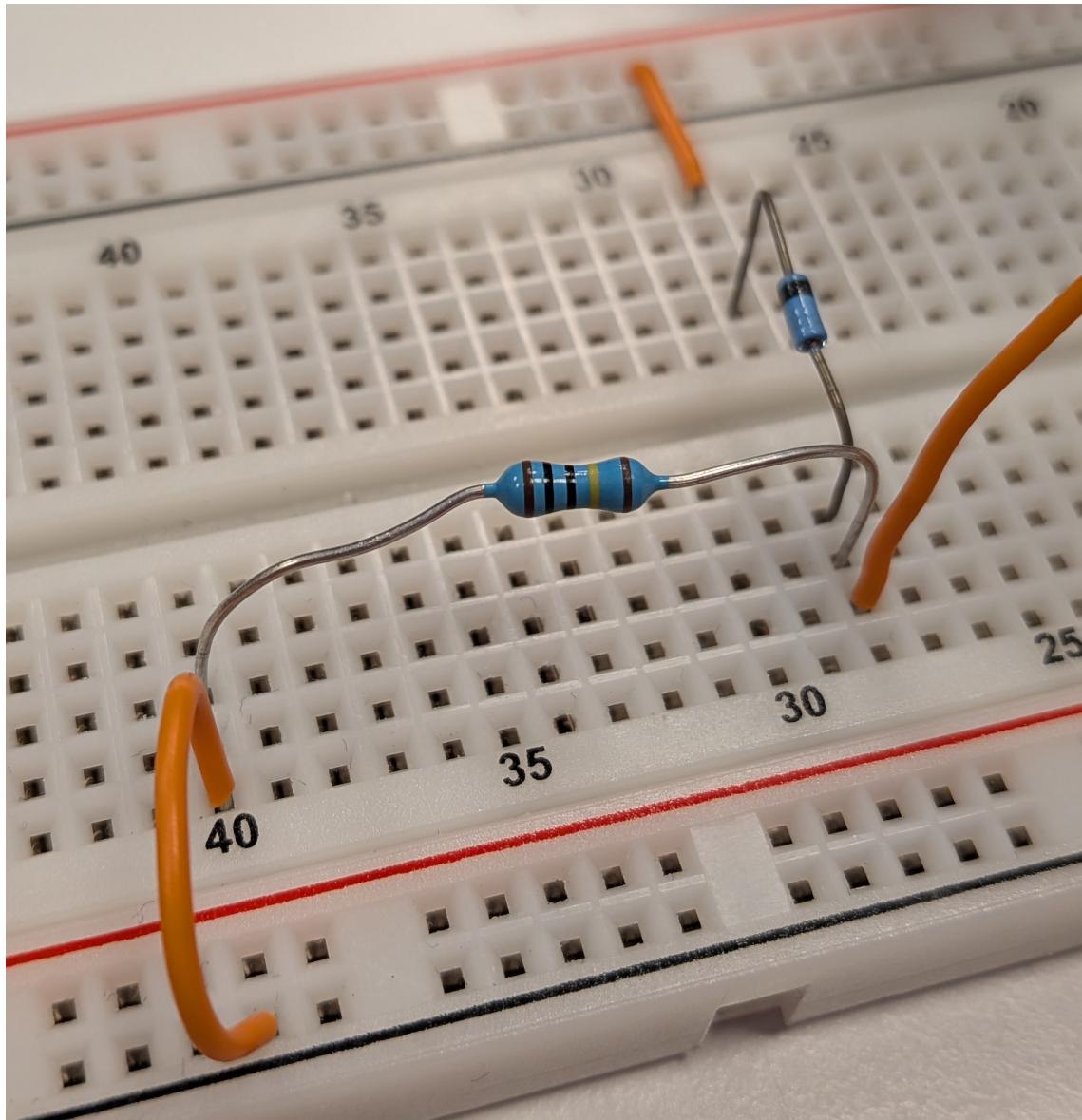


Figure 3.0: Part 3 circuit

Table 3.0: Reverse-bias measurements

$E$ (Measured)	20.03	V
$R_M$ (Assumed)	10	MΩ
$R$ (Measured)	1002.5	kΩ
$V_R$ (Measured)	6.2	mV
$I_S$ (Calculated)	6.805	nA
$R_{DC}$ (Calculated)	2942.71	MΩ

It looks as if the values for  $I_S$  and  $R_{DC}$  miss by an order of magnitude or two as the calculated reverse-bias resistance often leads to values between hunders of kΩ and up to a hundred MΩ. The inherent inaccuracies in the measurements are probably the cause of this magnitudinal error.

## 4. Part 4 - LED characteristics

This part is about testing the characteristics of LED's.

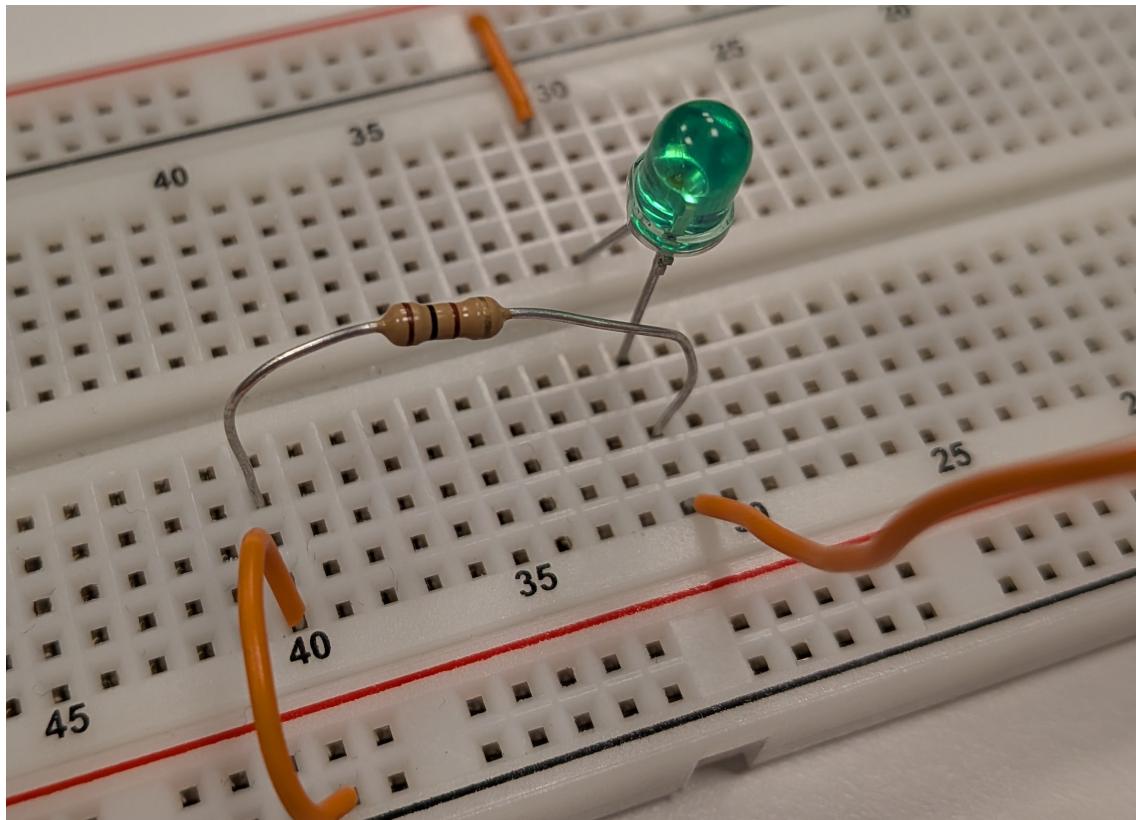


Figure 4.0: Part 4 circuit

First the circuit was connected and then the voltage supply was slowly ramped up. when first light appeared the value was recorded. Although hard to see, in Figure 4.1a there is a very faint sub-lumen light emitting from the diode. Then the supply was ramped up intill brightness leveled out at a bright level and values was recorded again.

Table 4.0: LED measurements

Measurements	First light	Bright
$V_D$ (Measured)	1.787 V	2.185 V
$V_R$ (Measured)	17.8 mV	3.632 V
$I_D$ (Calculated)	179.980 $\mu$ A	36.724 mA

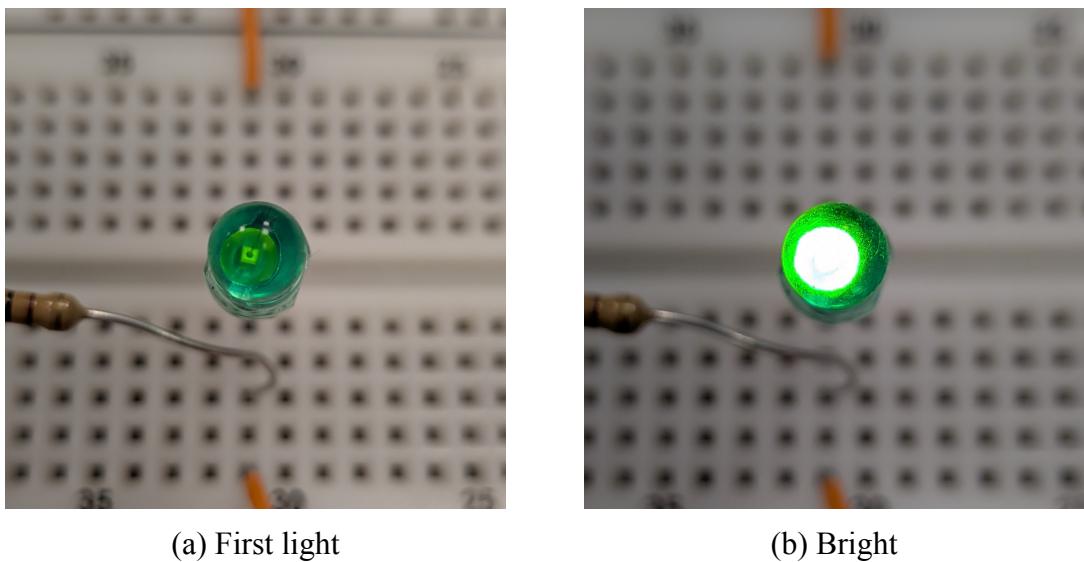


Figure 4.1: Part 4 circuit

Then multiple data points was collected for differnt input voltages, and the results are listed below in Tble 4.1 and then graphed.

Table 4.1: LED values

$E$ (V)	0.000	1.033	2.008	3.008	4.002	5.010	6.040
$V_D$ (V)	0.000	1.032	1.860	1.987	2.066	2.135	2.201
$V_R$ (V)	0.000	0.000	0.146	1.019	1.934	2.875	3.840
$I_D$ (mA)	0.000	0.000	1.480	10.303	19.555	29.070	38.827

## **5. Part 5 - Zener characteristics**